

Operational Amplifier Basics

As well as resistors and capacitors, Operational Amplifiers, or Op-amps as they are more commonly called, are one of the basic building blocks of Analogue Electronic Circuits.

Operational amplifiers are linear devices that have all the properties required for nearly ideal DC amplification and are therefore used extensively in signal conditioning, filtering or to perform mathematical operations such as add, subtract, integration and differentiation.

An Operational Amplifier, or op-amp for short, is fundamentally a voltage amplifying device designed to be used with external feedback components such as resistors and capacitors between its output and input terminals. These feedback components determine the resulting function or “operation” of the amplifier and by virtue of the different feedback configurations whether resistive, capacitive or both, the amplifier can perform a variety of different operations, giving rise to its name of “Operational Amplifier”.

An Operational Amplifier is basically a three-terminal device which consists of two high impedance inputs, one called the Inverting Input, marked with a negative or “minus” sign, (-) and the other one called the Non-inverting Input, marked with a positive or “plus” sign (+).

The third terminal represents the operational amplifiers output port which can both sink and source either a voltage or a current. In a linear operational amplifier, the output signal is the amplification factor, known as the amplifiers gain (A) multiplied by the value of the input signal and depending on the nature of these input and output signals, there can be four different classifications of operational amplifier gain.

Voltage – Voltage “in” and Voltage “out”

Current – Current “in” and Current “out”

Transconductance – Voltage “in” and Current “out”

Transresistance – Current “in” and Voltage “out”


Since most of the circuits dealing with operational amplifiers are voltage amplifiers, we will limit the tutorials in this section to voltage amplifiers only, (V_{in} and V_{out}).

The output voltage signal from an Operational Amplifier is the difference between the signals being applied to its two individual inputs. In other words, an op-amps output signal is the difference between the two input signals as the input stage of an Operational Amplifier is in fact a differential amplifier as shown below.

Differential Amplifier

The circuit below shows a generalized form of a differential amplifier with two inputs marked V_1 and V_2 . The two identical transistors TR_1 and TR_2 are both biased at the same operating point with their emitters connected together and returned to the common rail, $-V_{EE}$ by way of resistor R_E . The circuit operates

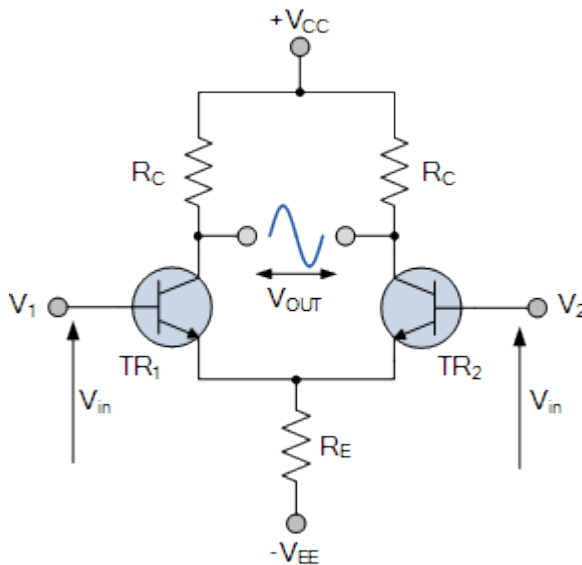from a dual supply $+V_{CC}$ and $-V_{EE}$ which ensures a constant supply. The voltage that appears at the output, V_{out} of the amplifier is the difference between the two input signals as the two base inputs are in anti-phase with each other.



So as the forward bias of transistor, TR_1 is increased, the forward bias of transistor TR_2 is reduced and vice versa. Then if the two transistors are perfectly matched, the current flowing through the common emitter resistor, R_E will remain constant.

Like the input signal, the output signal is also balanced and since the collector voltages either swing in opposite directions (anti-phase) or in the same direction (in-phase) the output voltage signal, taken from between the two collectors is, assuming a perfectly balanced circuit the zero difference between the two collector voltages.

This is known as the Common Mode of Operation with the common mode gain of the amplifier being the output gain when the input is zero.

Operational Amplifiers also have one output (although there are ones with an additional differential output) of low impedance that is referenced to a common ground terminal and it should ignore any common mode signals that is, if an identical signal is applied to both the inverting and non-inverting inputs there should no change to the output.


However, in real amplifiers there is always some variation and the ratio of the change to the output volt-

age with regards to the change in the common mode input voltage is called the Common Mode Rejection Ratio or CMRR.

Operational Amplifiers on their own have a very high open loop DC gain and by applying some form of Negative Feedback we can produce an operational amplifier circuit that has a very precise gain characteristic that is dependent only on the feedback used. Note that the term “open loop” means that there are no feedback components used around the amplifier so the feedback path or loop is open.

An operational amplifier only responds to the difference between the voltages on its two input terminals, known commonly as the “Differential Input Voltage” and not to their common potential. Then if the same voltage potential is applied to both terminals the resultant output will be zero. An Operational Amplifiers gain is commonly known as the Open Loop Differential Gain, and is given the symbol (A_o).

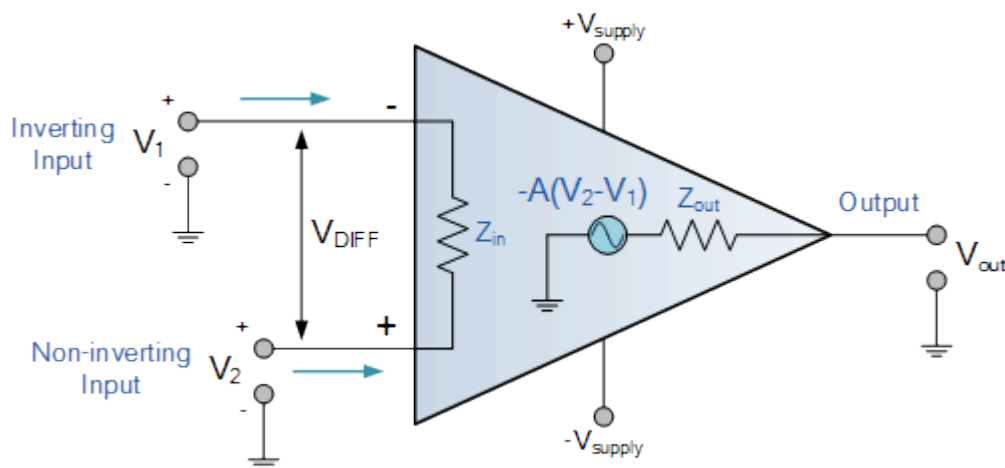Equivalent Circuit of an Ideal Operational Amplifier



Op-amp Parameter and Idealized Characteristic

Open Loop Gain, (A_{vo})